

Roll No. ....

Total No. of Questions : 07]

[Total No. of Pages : 02

## Paper ID [B0209]

(Please fill this Paper ID in OMR Sheet)

**BCA (Sem. - 2<sup>nd</sup>)****DIGITAL CIRCUITS AND LOGIC DESIGN (BC - 205)****Time : 03 Hours****Maximum Marks : 60****Instruction to Candidates:**

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.

### Section - A

**Q1)****(10 x 2 = 20)**

- a) What is the largest decimal number that can be represented by 16 bit binary word?
- b) What are the applications of binary number system?
- c) Convert the decimal number 39.75 to octal.
- d) How can you use NAND gate as inverter?
- e) Construct the truth table for  $F = xy + \bar{x}\bar{y}$ .
- f) What are maxterms?
- g) What is the difference between combinational and sequential circuits?
- h) What is a D-flip flop?
- i) What is priority encoder?
- j) Add a parity bit to make odd parity in the binary word 11001101.

**E-823 [1208]****P.T.O.**

**Section - B****(4 x 10 = 40)**

- Q2)** (a) Implement XOR gate using only NAND gates. What are its applications?  
(b) What are weighted codes? Give examples.
- Q3)** (a) Simplify the expression  $F = \bar{A}B(B + C) + BC(\bar{A} + \bar{B})$ .  
(b) State the De-Morgan's theorems. Draw the truth tables and equivalent logic circuits.
- Q4)** (a) Convert the given expression in canonical SOP form  $Y = AC + AB + BC$ .  
(b) Simplify the function using Karnaugh map and implement using minimum number of logic gates.  $F = \sum m(0, 2, 4, 7, 8, 13, 14)$
- Q5)** (a) Draw the logic diagram of full adder. Discuss its working.  
(b) What is the difference between a decoder and a demultiplexer? Draw the logic diagram of 1 to 8 decoder.
- Q6)** (a) What is the difference between level and edge triggering? Explain the working of master slave J-K flip flop.  
(b) Explain the basic principle of shift register. Describe the operation of parallel shift register.
- Q7)** (a) Differentiate between synchronous and asynchronous counters.  
(b) What is the limitation of parity method for error detection? Describe the Hamming code for error detection and correction.

