

Roll No.

Total No. of Questions : 07]

[Total No. of Pages : 02

BCA (Sem. - 2nd)
DIGITAL CIRCUIT AND LOGIC DESIGN
SUBJECT CODE : BC - 205 (N2)
Paper ID : [B0209]

[Note : Please fill subject code and paper ID on OMR]

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is Compulsory.
- 2) Attempt any Four questions from Section - B.

Section - A

Q1)

(10 × 2 = 20)

- a) Explain gate propagation delay time.
- b) What are the different minimization techniques?
- c) Reduce the following into SOP and POS form
 $\pi m(0, 1, 2, 3, 4, 6, 10, 11, 13)$ and $\Sigma m(0, 2, 4, 6, 10, 11, 12, 14, 15)$
- d) Explain Noise margin of a Logic circuit.
- e) Explain **Field Effect Transistor** as a Switch.
- f) What do you mean by Fan IN and Fan OUT for a digital circuit?
- g) What is the difference between Combinational circuit and sequential circuit?
- h) Convert $(0.6875)_{10}$ into octal.
- i) What do you mean by **non-weighted** codes?
- j) Define Character Codes.

Section - B

(4 × 10 = 40)

- Q2)** Minimize the following Boolean function using Quine-Mccluskey's methods and check with Karnaugh Map reduction method $f(A, B, C, D) = \Sigma (0, 1, 2, 3, 6, 7, 13, 14)$.

J-331[8129]

P.T.O.

Q3) Explain design of synchronous counters.

Q4) Explain code converters.

Q5) Explain Decoder for binary to gray code.

Q6) Write all possible groups of eight adjacent ones in a four variable k-map.

Q7) Explain up down and programmable counters.

*** * ***

a2zpapers.com