

Roll No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 07

**BCA (2011 & Onward) (Sem.-3)**  
**DIGITAL CIRCUITS AND LOGIC DESIGN**  
Subject Code : BSBC-303  
Paper ID : [B0230]

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTION TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and a student has to attempt any FOUR questions.

**SECTION - A**

1) Write briefly :

- a) What is Race condition?
  - b) Why universal Gate is called so?
  - c) What is Sequential circuit?
  - d) What is the use of complements?
  - e) What are Registers?
  - f) What is meant by Parity Bit?
  - g) What is XNOR gate?
  - h) Define Binary logic.
  - i) What are Decoders?
  - j) How to Convert Octal number to binary number? Give example.
-

## SECTION - B

- 2) What are Logic gates? Explain its types with diagram and applications.
- 3) What are K-Maps? Explain how an expression can be solved using K-Maps with suitable example.
- 4) Explain Multiplexer and De-Multiplexer with diagram.
- 5) What are uses of Asynchronous counters? Explain the working of asynchronous counter by giving any counter of your choice.
- 6) Explain the following :
  - a) SOP form
  - b) Binary Adder
- 7) What is Boolean Algebra? Write basic identities of Boolean Algebra. Explain the role of DeMorgan's theorem in Boolean Algebra.

a2zpapers.com