

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 07

BCA (2011 & Onward) (Sem.-3)
DIGITAL CIRCUITS AND LOGIC DESIGN
Subject Code : BSBC-303
Paper ID : [B0230]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and a student has to attempt any FOUR questions.

SECTION-A**1. Write briefly :**

- a) Define Gates. Give the truth table of XOR gate.
 - b) Define K Mapping. a2zpapers.com
 - c) $(3A.2F)_{16} = ()_{10}$
 - d) 1's and 2's complement of (10101110)
 - e) Perform the following :
 $(11001101) + (01011100)$
 - f) What are Mod N counters?
 - g) What is Latch?
 - h) Give Idempotent Law.
 - i) Define Data Selector.
 - j) Give truth table of Full Adder.
-

SECTION-B

- 2) a) Subtract $(11010)_2$ from $(11101)_2$ using 2's complement Method.
b) What is Race Around Condition?
- 3) a) Simply using K Mapping.
b) Why NAND and NOR are called Universal Gates?
- 4) Explain the working of JK Flip Flop.
- 5) Explain 4 bit Parallel binary Adder with example?
- 6) a) Difference between Multiplexer and Demultiplexer.
b) Draw circuit of 3:8 line decoder.
- 7) Explain the working of 4 bit Ripple Counter.

a2zpapers.com