

Roll No.

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

Total No. of Pages : 02

Total No. of Questions : 07

B.Sc.(IT) (2015 Batch) (Sem.-2)
DIGITAL CIRCUIT AND LOGIC DESIGN
Subject Code : BSIT-204
Paper ID : [72727]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and students have to attempt any FOUR questions.

SECTION-A**1. Write briefly :**

- i. Write the truth table of XNOR gate.
- ii. What are universal gates?
- iii. List two important applications of logic gates.
- iv. Define commutative law.
- v. What is absorption law?
- vi. What is minterm?
- vii. Define latch.
- viii. Differentiate between a latch and a flip flop.
- ix. What is race condition?
- x. What is shift register?

SECTION-B

2.
 - a. Convert $(0.6875)_{10}$ to binary. Show the steps involved.
 - b. Find the octal equivalent of $(100.250)_{10}$. show the steps involved.
3.
 - a. Prove that NAND is not associative.
 - b. Simplify the following Boolean function using K-maps :

$$F = \overline{A}\overline{B}\overline{C} + \overline{B}C\overline{D} + \overline{A}BC\overline{D} + A\overline{B}\overline{C}$$

4. Design the circuits for half adder and full adder and explain the steps involved.
5. Explain the design and working principles of R-S and J-K flip flops.
6.
 - a. Explain the excitation table of a flip flop.
 - b. What is a multivibrator? Explain its use in brief.
7. Convert the modulo-4 ripple counter to a synchronous counter.

a2zpapers.com