

Roll No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 07

**B.Sc.(IT) (Sem.-2)**  
**DIGITAL ELECTRONICS FUNDAMENTALS**  
Subject Code : BS-102  
Paper ID : [B0405]

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTION TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and a student has to attempt any FOUR questions.

**SECTION-A****Q1. Write briefly :**

- a) Convert  $(1046.25)_{10}$  into  $(?)_{16}$
  - b) Perform binary subtraction using 2's complement :  $36 - 47$
  - c) Explain Minterms and Maxterms.
  - d) What do you mean by Universal Gate?
  - e) Explain the LATCH by drawing the logical diagram.
  - f) What do you mean by Shift Register?
  - g) Differentiate between bit, byte and word.
  - h) What is Access Time?
  - i) What is Bipolar RAM cell?
  - j) What is Unicode?
-

**SECTION-B**

Q2) Write short note on :

- a) Weighted codes
- b) Self complementary codes
- c) Cyclic codes

Q3) Simplify the Boolean expression  $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$  in

- a) Sum of Product form
- b) Product of Sum form

Q4) Implement the following Boolean functions using OR-AND-INVERT Gate

$$F = (\bar{A} + \bar{B})(A+C)(A+D)$$

Q5) Design a 6\*32 Decoder with the help of 3\*8 decoders.

Q6) Explain 4-bit synchronous counter by drawing logical diagram.

Q7) Discuss in detail classification and characteristics of memories.