

Roll No.

Total No. of Questions : 09]

[Total No. of Pages : 03

B.Tech. (Sem. - 2nd)

BASIC ELECTRICAL & ELECTRONICS ENGINEERING

SUBJECT CODE : EE - 101Paper ID : [A0117]

[Note : Please fill subject code and paper ID on OMR]

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is Compulsory.
- 2) Attempt any Five questions from Section - B & C.
- 3) Select atleast Two questions from Section - B & C.

Section - A

Q1)

(Marks : 2 Each)

- a) Plot the fully labelled input - output characteristics of a typical thermistor.
- b) Differentiate between analog and digital electronics. Discuss the significance of binary number system in digital electronics.
- c) Differentiate between linear and digital ICs. Also give two examples of each.
- d) Draw a neat comparison between a JFET and MOSFET.
- e) In what respect an LED and a Zener diode are different from an ordinary PN junction diode?
- f) What is the role of deflecting and opposing torque in indicating instruments?
- g) What is the need of starter in dc motor?
- h) State and explain Kirchhoff's laws.
- i) In a circuit, the applied voltage of 150 V lags the current 8A by 40°. Determine
 - (i) Is the power factor lagging or leading?
 - (ii) What is value of power factor.
 - (iii) Is the circuit inductive or capacitive?
 - (iv) What is value of active and reactive power?
- j) Calculate the admittance $G + jB$, if the impedance is $10 + j5$ ohms.


R-1266

P.T.O.

Section - B

(Marks : 8 Each)

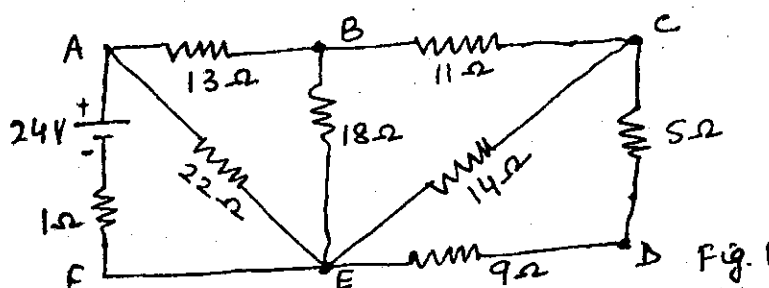- Q2) (a) An aluminium wire 10 m long and 2 mm in diameter is connected in parallel to a copper wire 6 m long. A total of 2 A is passed through the combination and it is seen that the current through aluminium wire is 1.25 A. Calculate the diameter of copper wire. Specific resistance of copper is $1.6 \times 10^{-6} \Omega \text{ cm}$ and that of aluminium is $2.6 \times 10^{-6} \Omega \text{ cm}$.
- (b) An electrical network is arranged as shown in Fig 1.
- Find the current in branch AF,
 - Power absorbed in branch BE and
 - Potential difference across branch CD.



- Q3) (a) Derive the expression for resonant frequency and Q factor for a series resonant RLC circuit.
- (b) A coil of resistance 15 ohms and inductance 0.05H is connected in parallel with non - inductive resistor of 20 ohms. Find
- The current in each branch and total current supplied, and
 - The phase angle of the combination when a voltage of 200 V at 50Hz is applied. Draw the phasor diagram.
- Q4) (a) Why is damping torque necessary in indicating instruments? Explain with neat sketches different methods of producing the same.
- (b) Differentiate between moving coil and moving iron measuring instruments.

Q5) Describe the principle, construction and working of 3- phase induction motor with neat diagrams.

Section - C

(Marks : 8 Each)

Q6) (a) Define a transducer. List the various application areas of transducer based systems.

(b) Describe the construction, working principle and limitations of bonded type metallic strain gauges.

Q7) (a) Describe the working of a NOR gate based R-S flip - flop. What is its limitation? How does JK flip - flop overcome it?

(b) Convert $4ABC_{16}$ into its equivalent octal and decimal number system.

(c) Realize XOR gate using NAND gates.

Q8) (a) Describe the pin configuration and internal block description of IC -555.

(b) What is a voltage regulator? Describe the working and specifications of any regulator IC.

Q9) (a) Describe the amplifying action of a transistor.

(b) What is a Thyristor? Explain its working and V - I characteristics.

